

# **Understanding LITELINK™ Display Feature Signal Routing and Applications**

## 1. Introduction

This application note further explains the display feature (often called caller-ID or CID) signal routing functions of the LITELINK Phone Line Interface (DAA).

## 2. $\overline{\text{CID}}$ Input Operation

$\overline{\text{CID}}$  is an active-low input to LITELINK that changes internal signal routing on the chip. The  $\overline{\text{CID}}$  input has an internal pull-up resistor that keeps the input deasserted when not in use.

With  $\overline{\text{CID}}$  asserted, the  $\overline{\text{RING}}$  output of LITELINK is disabled. Signals, including ringing signals, on the snoop path are coupled to the RX+/RX- outputs. These signals are affected by the high-pass effect of the snoop capacitors.

With  $\overline{\text{CID}}$  deasserted and  $\overline{\text{OH}}$  asserted, signals on the line are coupled to the RX+/RX- outputs through the optical link on the LITELINK. Signals on the snoop path are not coupled to the RX+/RX- outputs when  $\overline{\text{CID}}$  is deasserted.

## 3. Applications of $\overline{\text{CID}}$

### 3.1 Display Feature Burst Prior to Ringing

For applications where the display feature signal burst precedes the first ringing burst, many designers choose the following operating procedure:

1. Assert  $\overline{\text{CID}}$  at all times when the LITELINK is on-hook.
2. Detect ringing via an external optocoupler or through the snoop path.
3. After reception of the display feature signal burst and verification of ringing, deassert  $\overline{\text{CID}}$ .

### 3.2 Display Feature Burst Between First and Second Ring

For applications where the display feature signal burst occurs between the first and second ringing bursts, many designers choose to deassert  $\overline{\text{CID}}$  until a ring signal can be verified on the  $\overline{\text{RING}}$  output using an operating sequence such as:

1. Deassert  $\overline{\text{CID}}$  in on-hook quiescent state.
2. On verification of ringing on  $\overline{\text{RING}}$ , assert  $\overline{\text{CID}}$ .
3. After the display feature burst time, deassert  $\overline{\text{CID}}$ .

## 4. For More Information

Clare Application Note AN-140, [Understanding LITELINK II](#) includes a truth table for LITELINK signal routing inputs in section 4.1.

## 5. LITELINK Design Resources

### 5.1 Clare, Inc. Design Resources

LITELINK datasheets and reference designs

Application note AN-114 ITC117P

Application note AN-117 [Customize Caller-ID Gain and Ring Detect Voltage Threshold for CPC5610/11](#)

Application note AN-140, [Understanding LITELINK II](#)

Application note AN-146, [Guidelines for Effective LITELINK Designs](#)

Application note AN-149, [Increased LITELINK II Transmit Power](#)

Application note AN-150, [Ground-start Supervision Circuit Using IAA110](#).

Application Note AN-152, [LITELINK II to LITELINK III Design Conversion](#)

## 5.2 Third Party Design Resources

The following also contain information useful for DAA designs. All of the books are available on [amazon.com](http://amazon.com).

*Understanding Telephone Electronics*, Stephen J. Bigelow, et. al., Butterworth-Heinemann; ISBN: 0750671750

*Newton's Telecom Dictionary*, Harry Newton, CMP Books; ISBN: 1578200695

*Photodiode Amplifiers: Op Amp Solutions*, Jerald Graeme, McGraw-Hill Professional Publishing; ISBN: 007024247X

Teccor, Inc. Surge Protection Products

*United States Code of Federal Regulations*, CFR 47 Part 68.3

For additional information please visit our website at: [www.ixysic.com](http://www.ixysic.com)

---

IXYS Integrated Circuits Division makes no representations or warranties with respect to the accuracy or completeness of the contents of this publication and reserves the right to make changes to specifications and product descriptions at any time without notice. Neither circuit patent licenses nor indemnity are expressed or implied. Except as set forth in IXYS Integrated Circuits Division's Standard Terms and Conditions of Sale, IXYS Integrated Circuits Division assumes no liability whatsoever, and disclaims any express or implied warranty, relating to its products including, but not limited to, the implied warranty of merchantability, fitness for a particular purpose, or infringement of any intellectual property right.

The products described in this document are not designed, intended, authorized or warranted for use as components in systems intended for surgical implant into the body, or in other applications intended to support or sustain life, or where malfunction of IXYS Integrated Circuits Division's product may result in direct physical harm, injury, or death to a person or severe property or environmental damage. IXYS Integrated Circuits Division reserves the right to discontinue or make changes to its products at any time without notice.

---

Specification: AN-155-R02  
©Copyright 2014, IXYS Integrated Circuits Division  
All rights reserved. Printed in USA.  
4/14/2014